


Pipelined RISC-V Processor

Pipelined RISC-V Processor


- **Temporal parallelism**
- Divide single-cycle processor into **5 stages**:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add **pipeline registers** between stages

Single-Cycle vs. Pipelined Processor


Single-Cycle

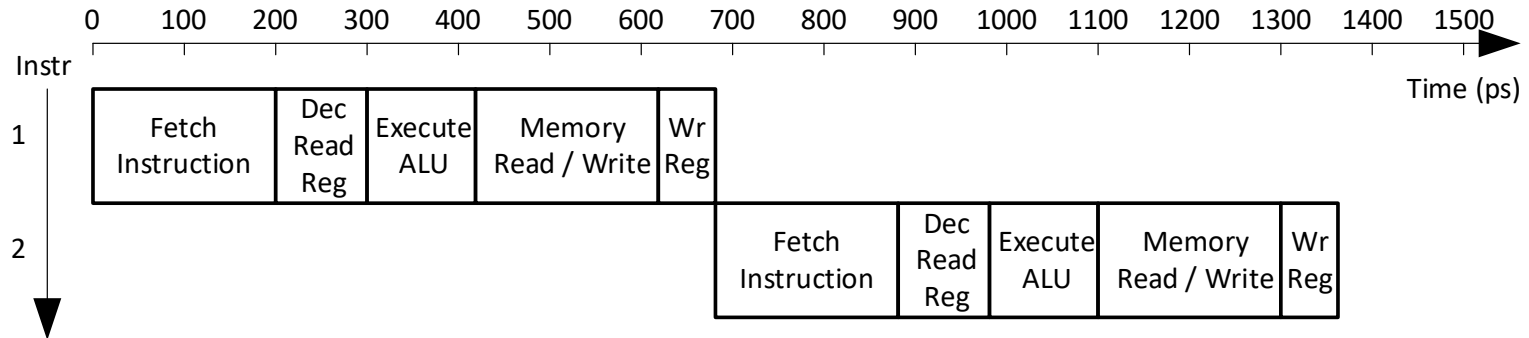



Pipelined

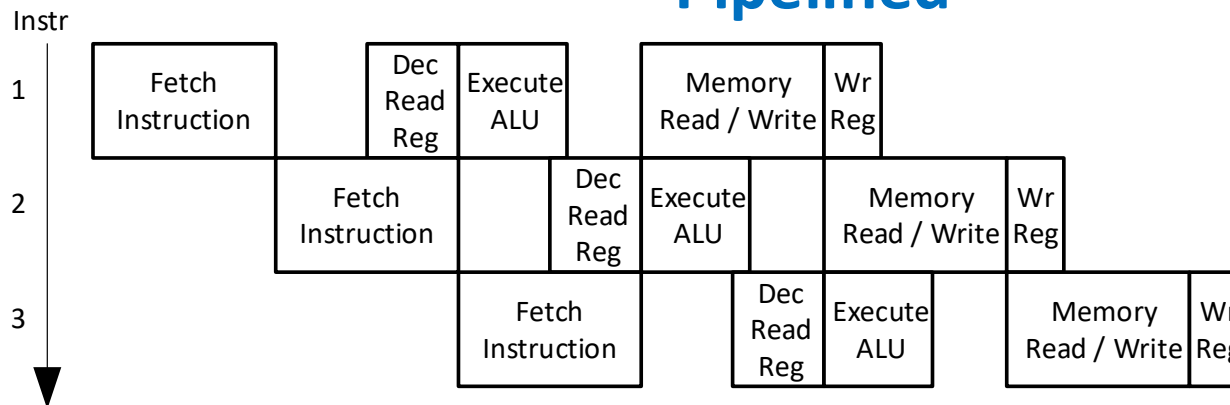

Pipelined Processor Abstraction

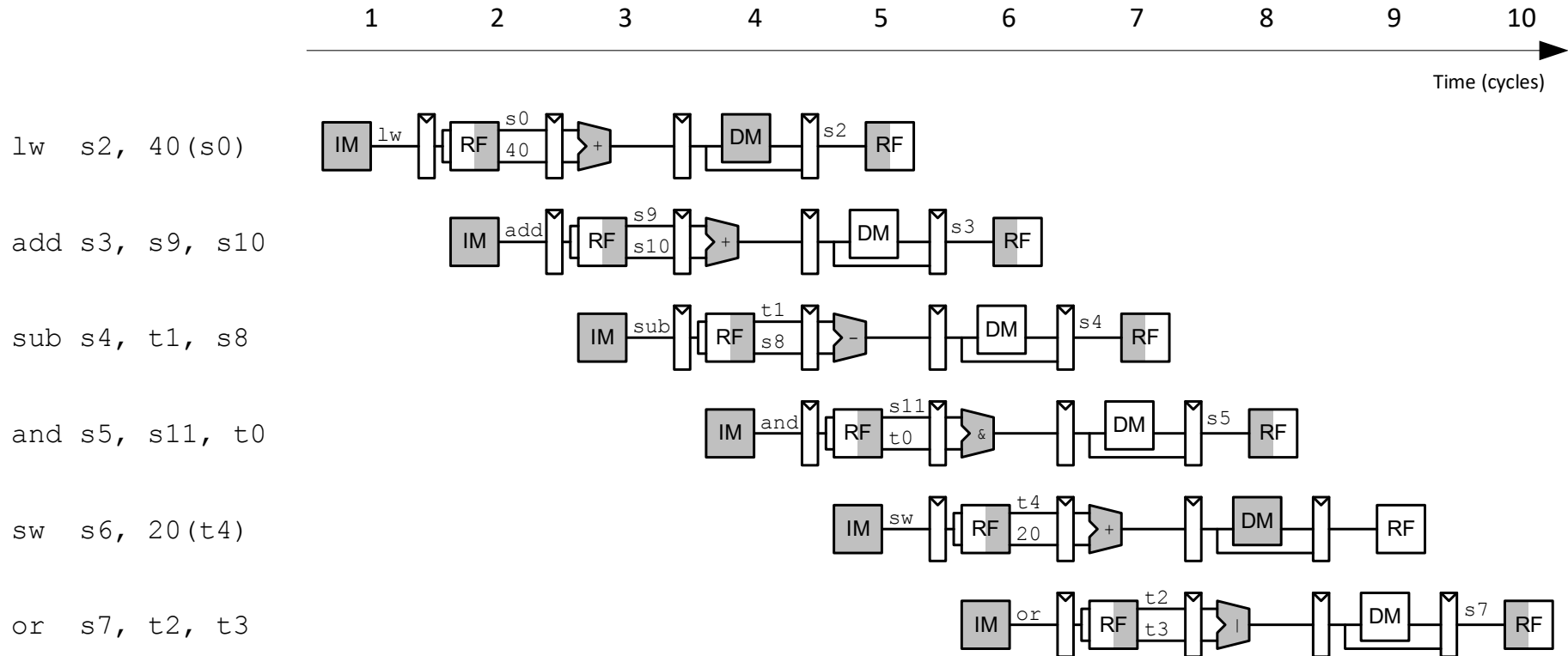


Single-Cycle & Pipelined Datapaths

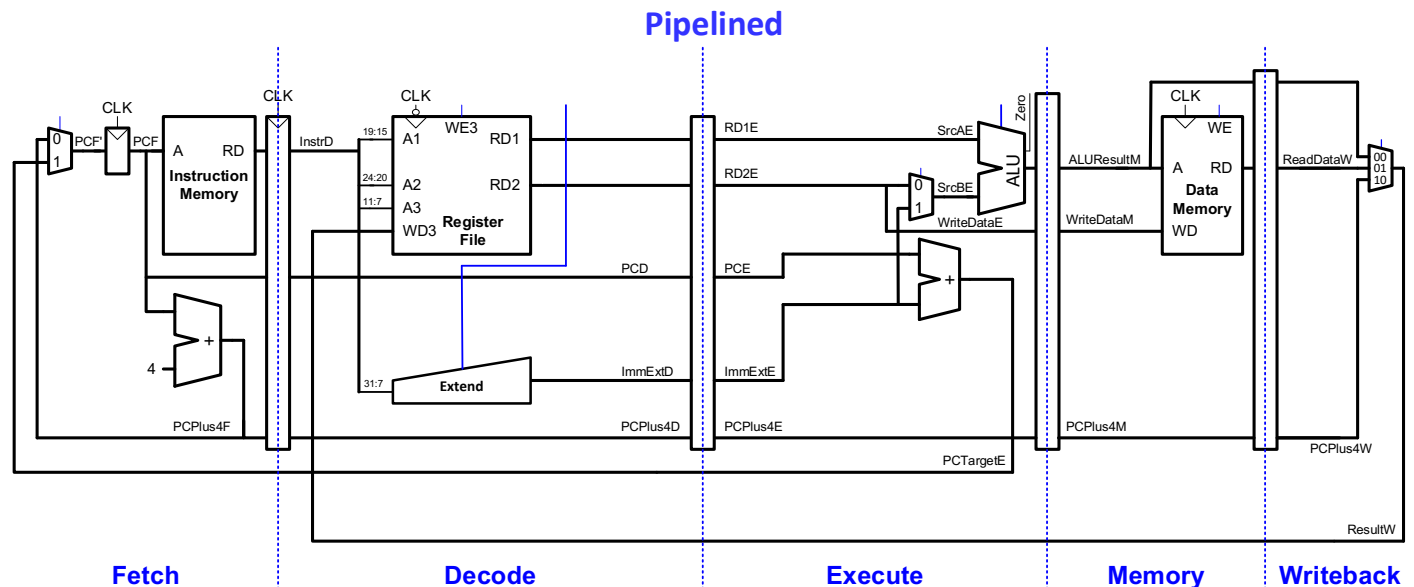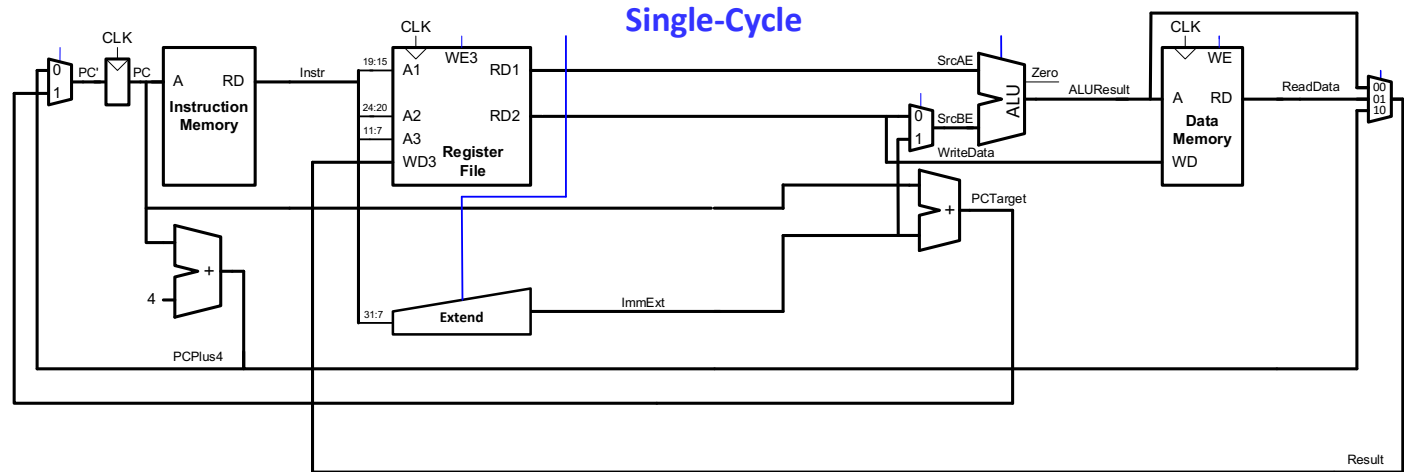


Signals in Pipelined Processor are appended with first letter of stage (i.e., PC**F**, PC**D**, PC**E**).

Corrected Pipelined Datapath

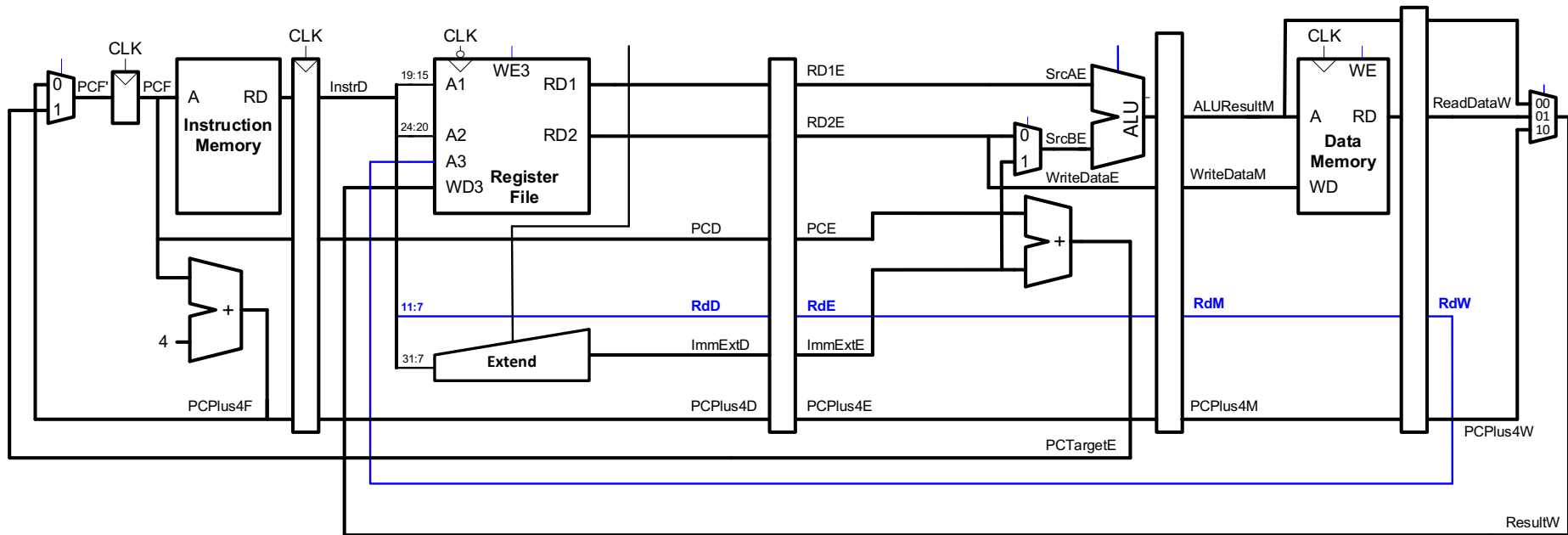

- ***Rd*** must arrive at same time as ***Result***
- Register file written on **falling edge** of *CLK*

Pipelined Processor with Control

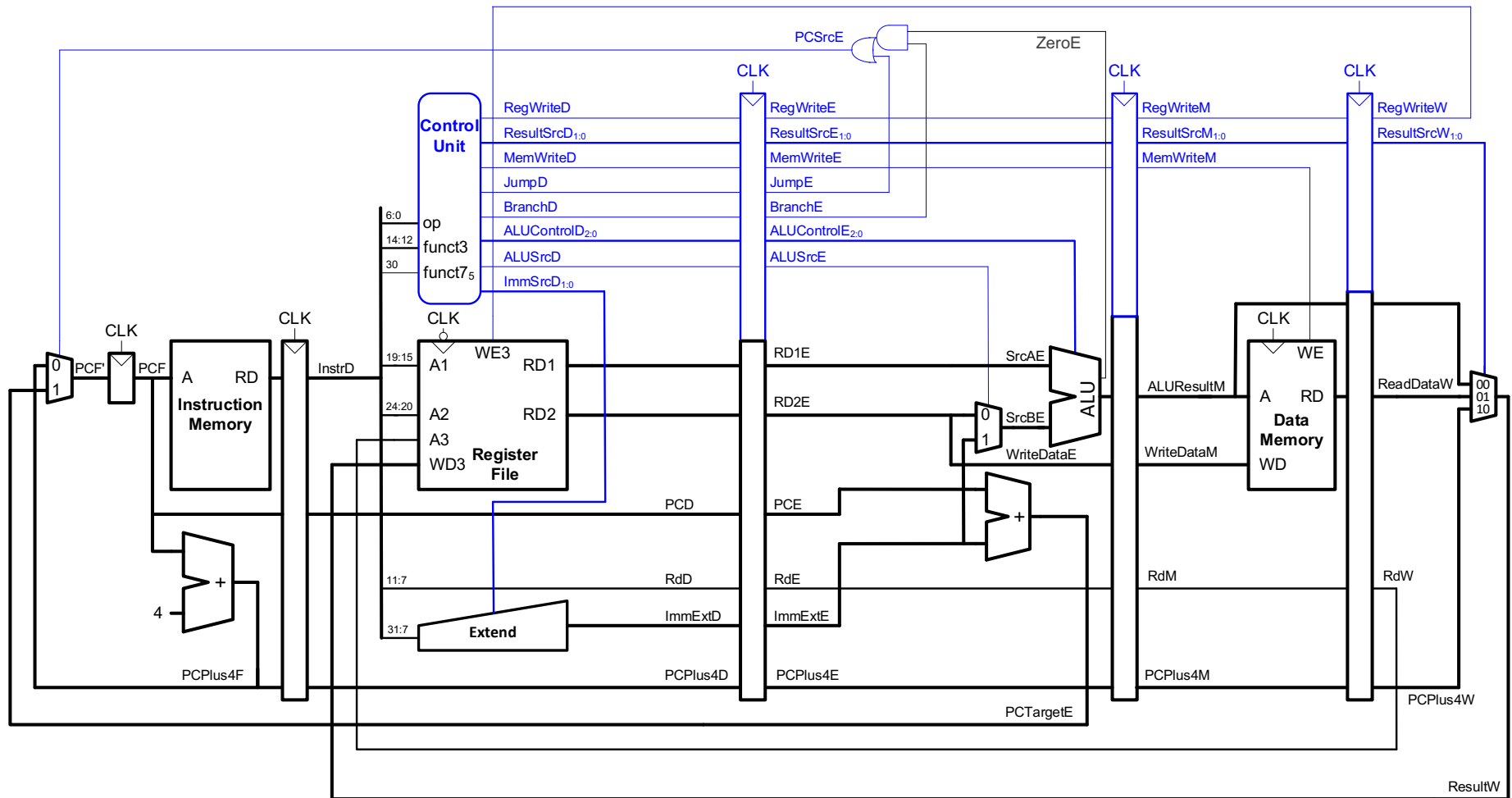


- **Same control unit** as single-cycle processor
- **Control signals travel with** the instruction (drop off when used)

Pipelined Processor Hazards

Pipelined Hazards


- When an instruction depends on result from instruction that hasn't completed
- Types:
 - **Data hazard:** register value not yet written back to register file
 - **Control hazard:** next instruction not decided yet (caused by branch)

Data Hazard

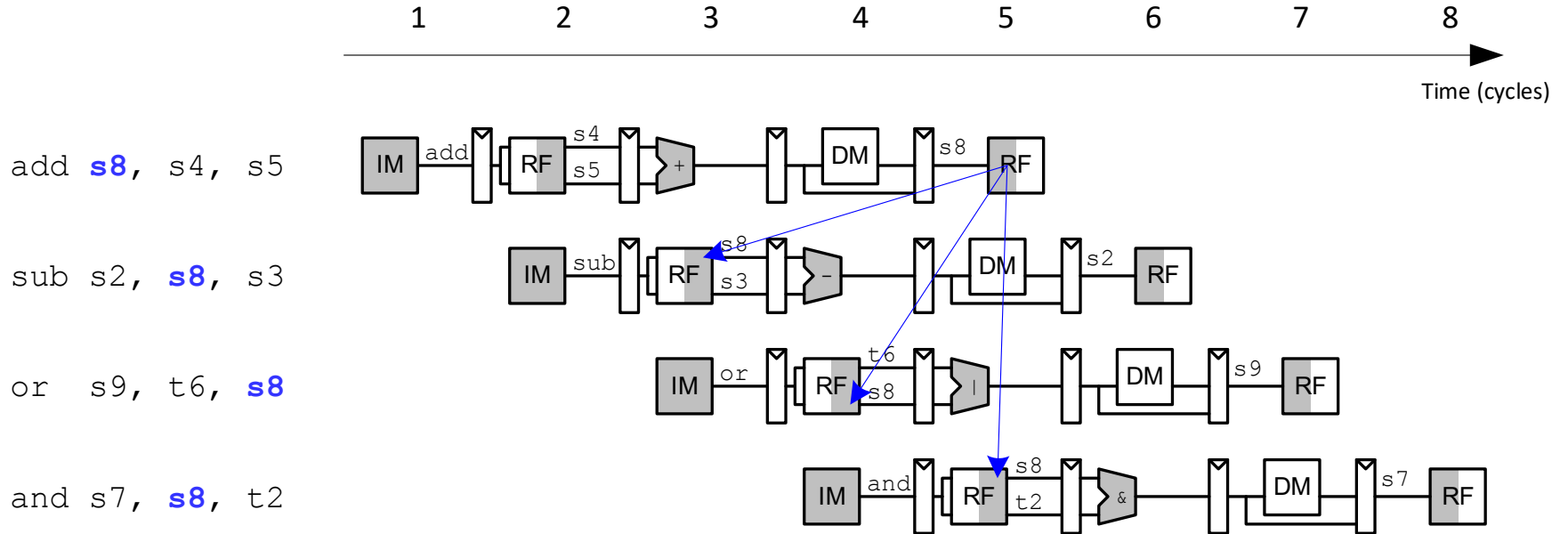


Handling Data Hazards

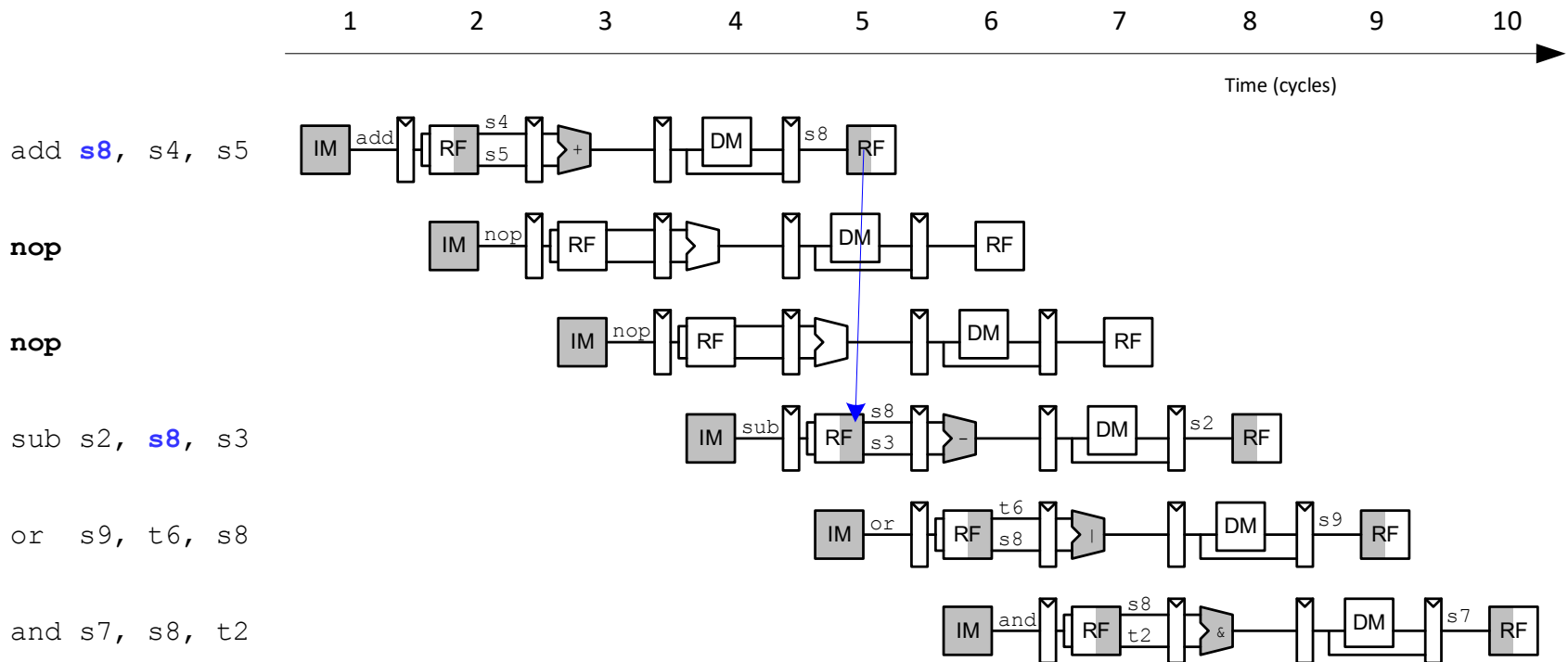- **Insert** enough **nops** for result to be ready
- Or move independent useful instructions forward




Data Forwarding

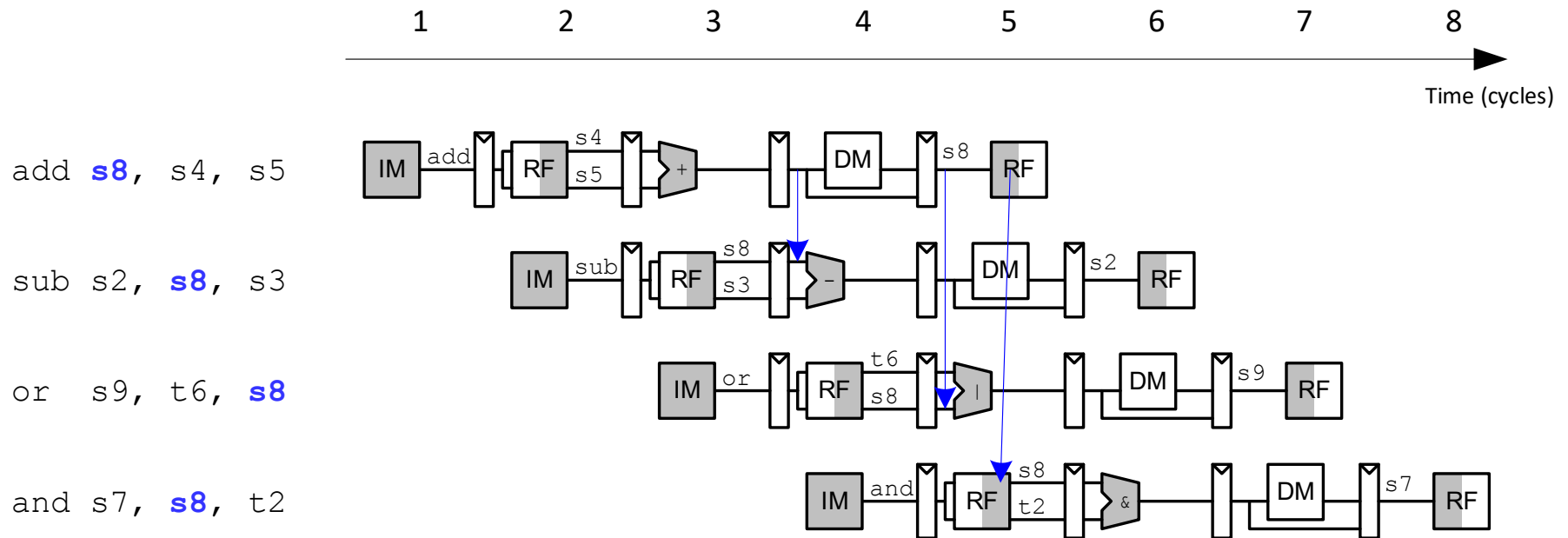- Data is **available on internal busses** before it is written back to the register file (RF).
- **Forward data** from internal busses **to Execute stage**.




Data Forwarding

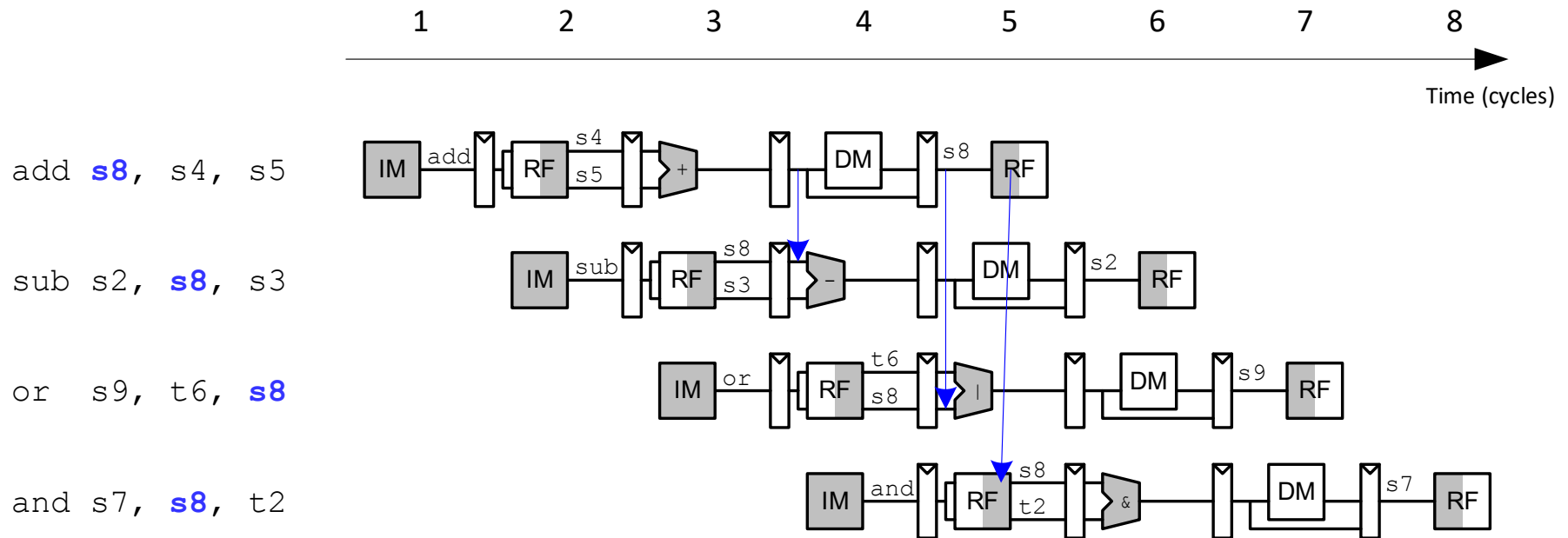- Check if source register **in Execute stage matches** destination register of instruction **in Memory or Writeback stage**.
- If so, forward result.



Data Forwarding: Hazard Unit

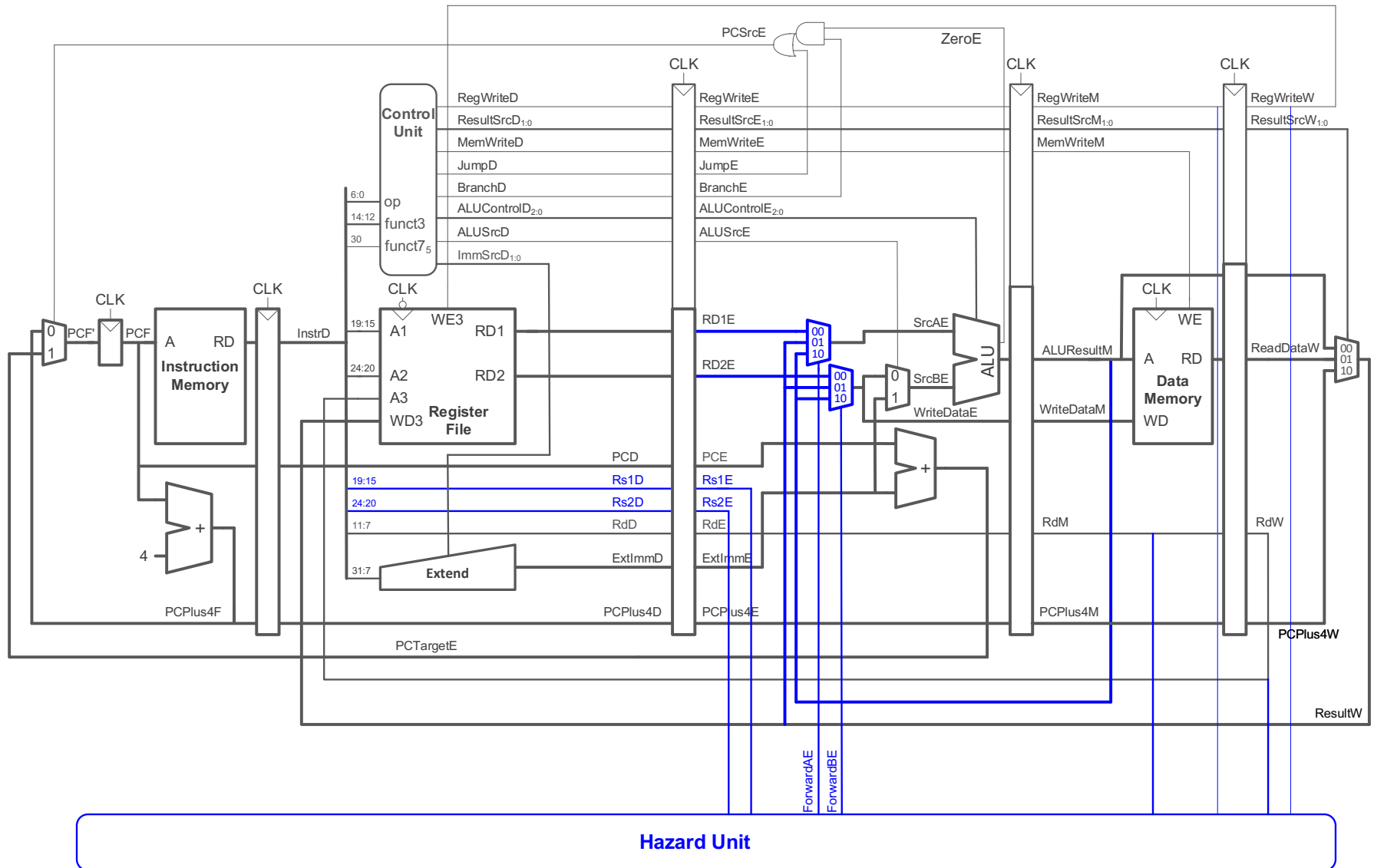

Data Forwarding

- **Case 1:** **Execute** stage $Rs1$ or $Rs2$ matches **Memory** stage Rd ?
Forward from Memory stage
- **Case 2:** **Execute** stage $Rs1$ or $Rs2$ matches **Writeback** stage Rd ?
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for $Rs1$:

```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ )           // Case 1
         $ForwardAE = 10$ 
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ )           // Case 2
         $ForwardAE = 01$ 
else     $ForwardAE = 00$                            // Case 3
```

***ForwardBE** equations are similar (replace $Rs1E$ with $Rs2E$)*

Data Forwarding


- **Case 1:** Execute stage $Rs1$ or $Rs2$ matches **Memory** stage Rd ?
Forward from Memory stage
- **Case 2:** Execute stage $Rs1$ or $Rs2$ matches **Writeback** stage Rd ?
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for $Rs1$:


```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ ) AND ( $Rs1E != 0$ ) // Case 1
        ForwardAE = 10
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ ) AND ( $Rs1E != 0$ ) // Case 2
        ForwardAE = 01
else    ForwardAE = 00                                     // Case 3
```

ForwardBE equations are similar (replace $Rs1E$ with $Rs2E$)

Data Hazard due to lw Dependency

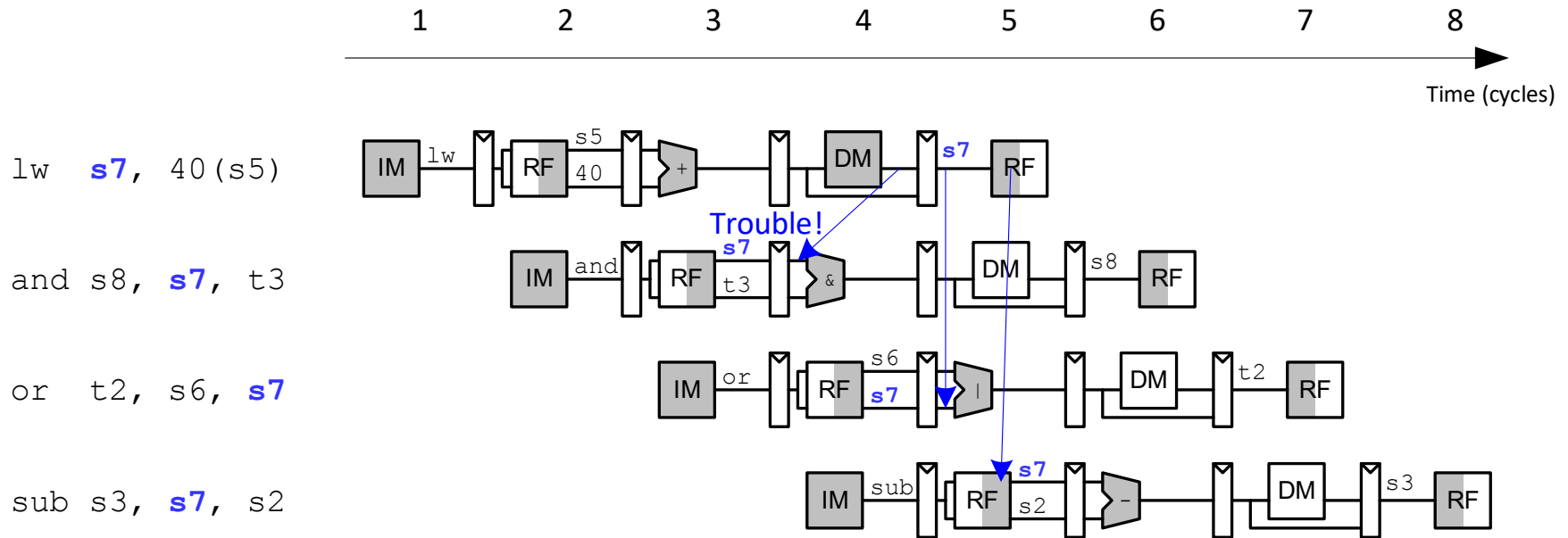

Stalling to solve 1w Data Dependency

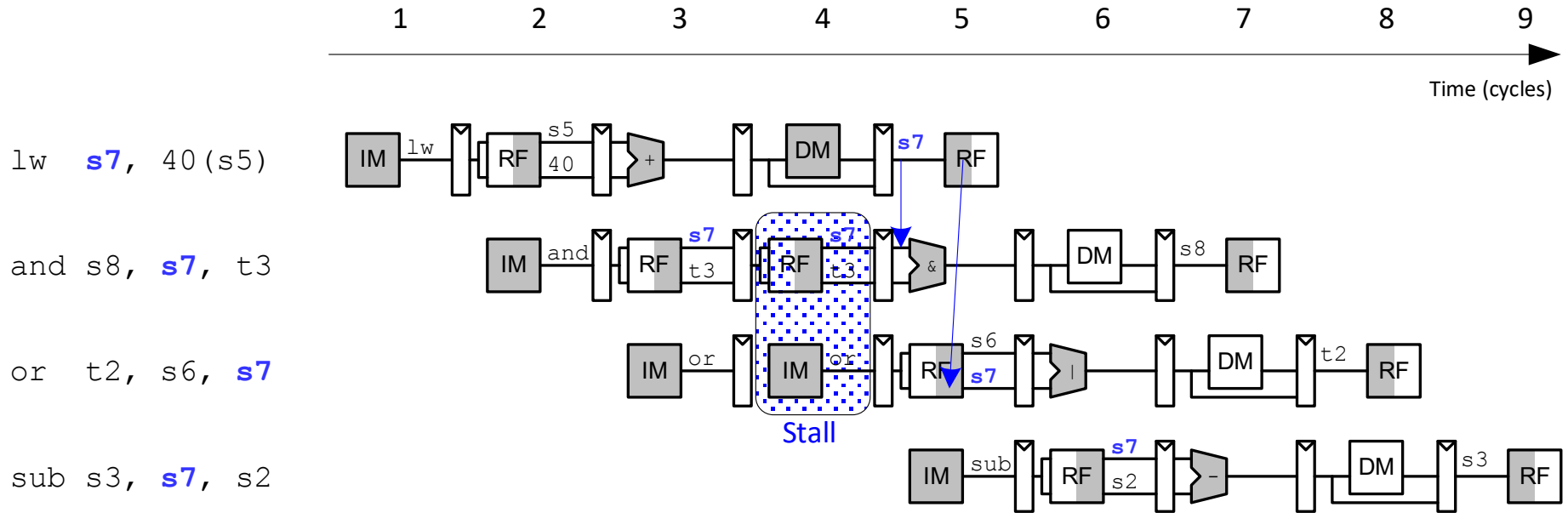

Stalling Logic

- Is either **source register in the Decode stage** the same as the **destination register in the Execute stage**?

AND


- Is the instruction in the **Execute stage a lw**?

$lwStall = ((Rs1D == RdE) \text{ OR } (Rs2D == RdE)) \text{ AND } ResultSrcE_0$

$StallF = StallD = FlushE = lwStall$

(Stall the Fetch and Decode stages, and flush the Execute stage.)

Stalling Hardware

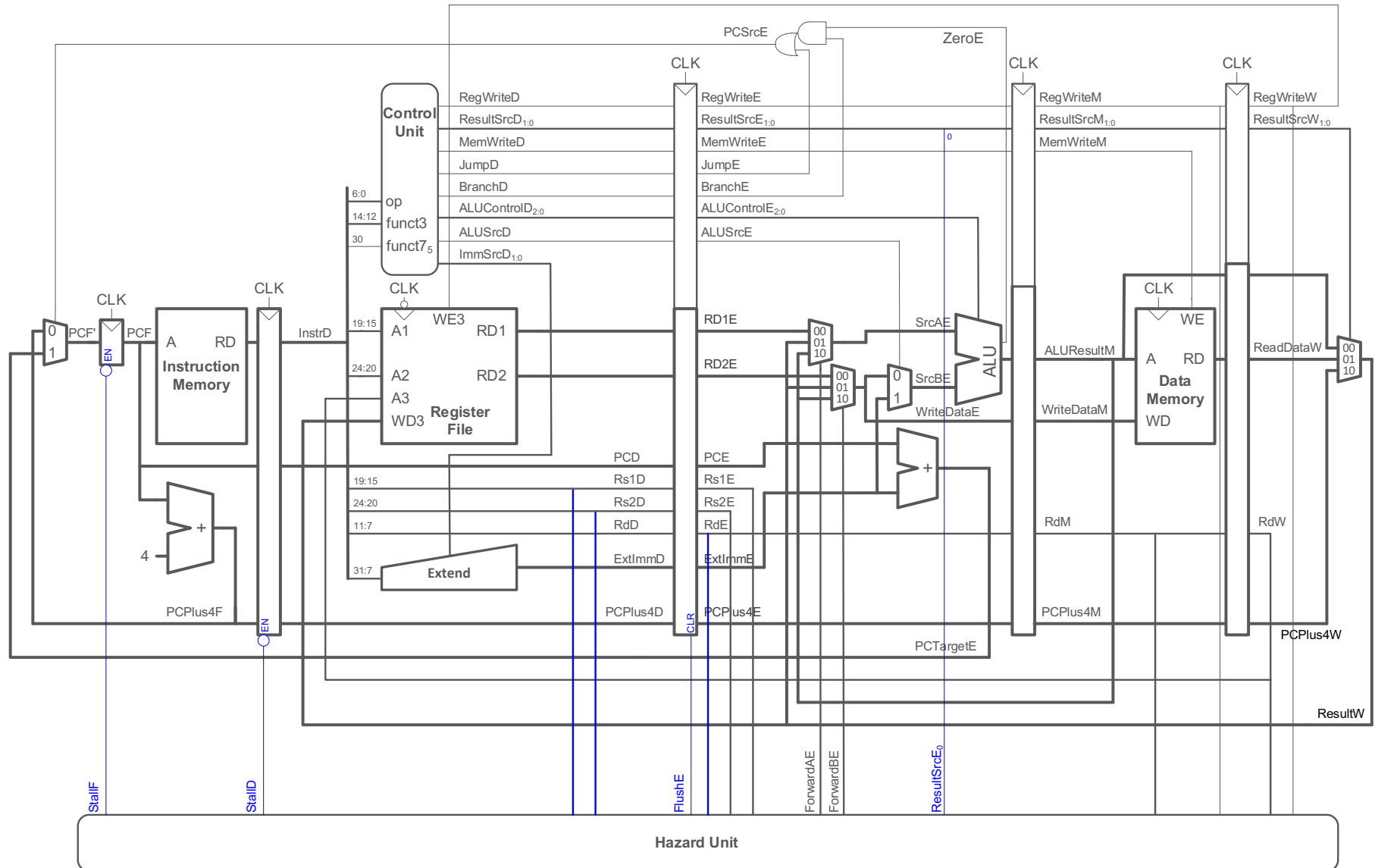


Pipelined Processor Control Hazards

Control Hazards

- **beq:**
 - Branch **not determined until the Execute stage** of pipeline
 - **Instructions** after branch **fetch** before branch occurs
 - These **2 instructions must be flushed** if branch happens

Control Hazards

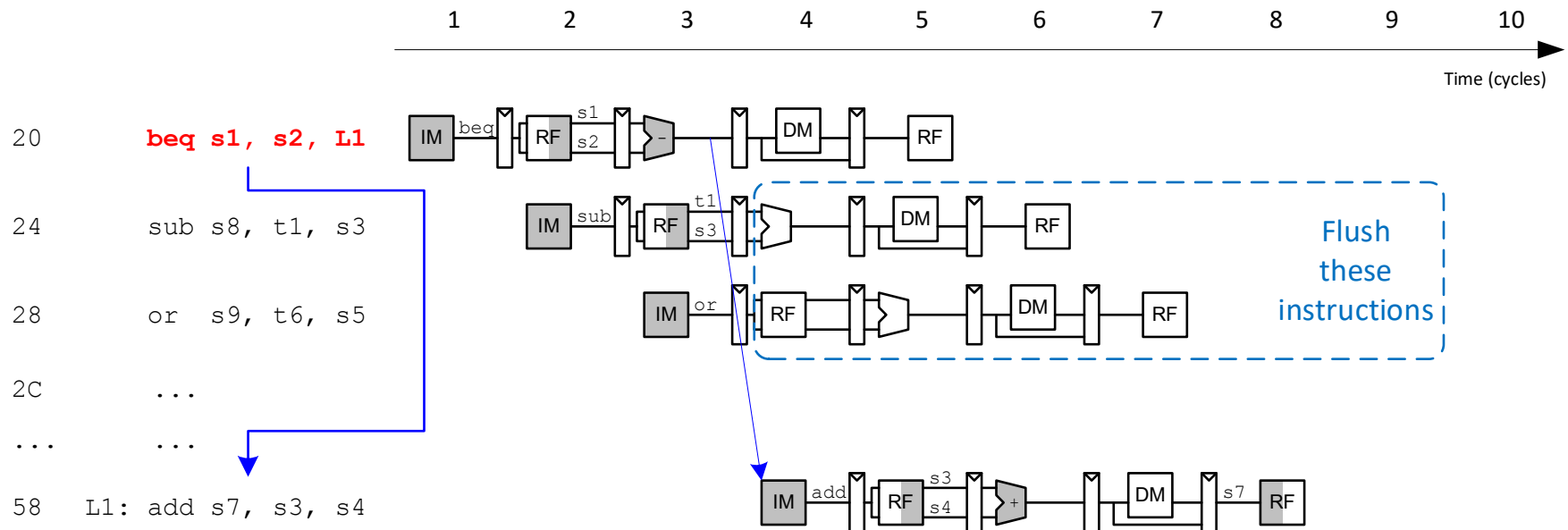

Branch misprediction penalty:

The number of instructions flushed when a branch is taken (in this case, 2 instructions)


Control Hazards: Flushing Logic

- If branch is taken in execute stage, need to flush the instructions in the Fetch and Decode stages
 - Do this by clearing Decode and Execute Pipeline registers using *FlushD* and *FlushE*
- **Equations:**


$$FlushD = PCSrcE$$

$$FlushE = lwStall \text{ OR } PCSrcE$$

Control Hazards: Flushing Hardware

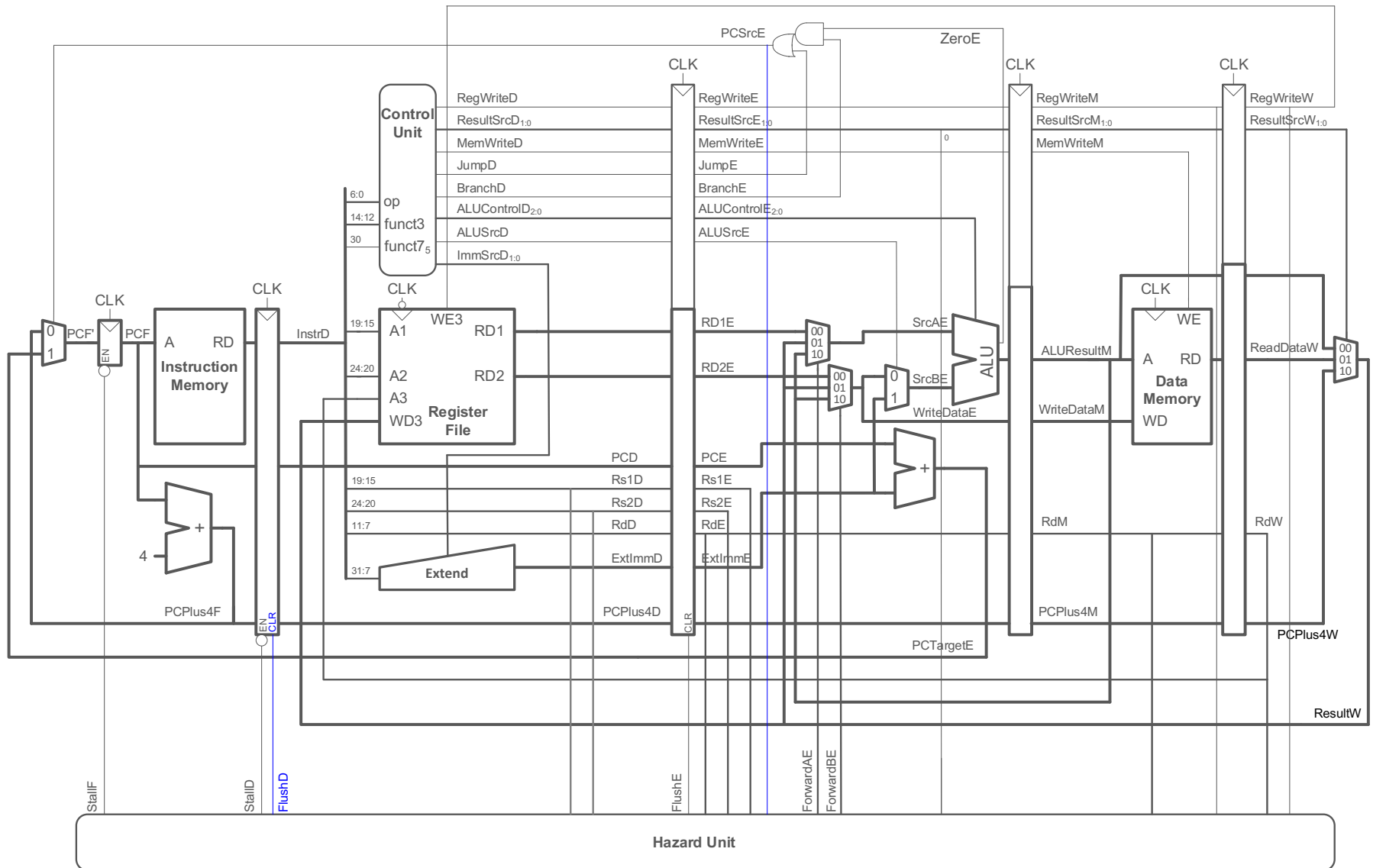

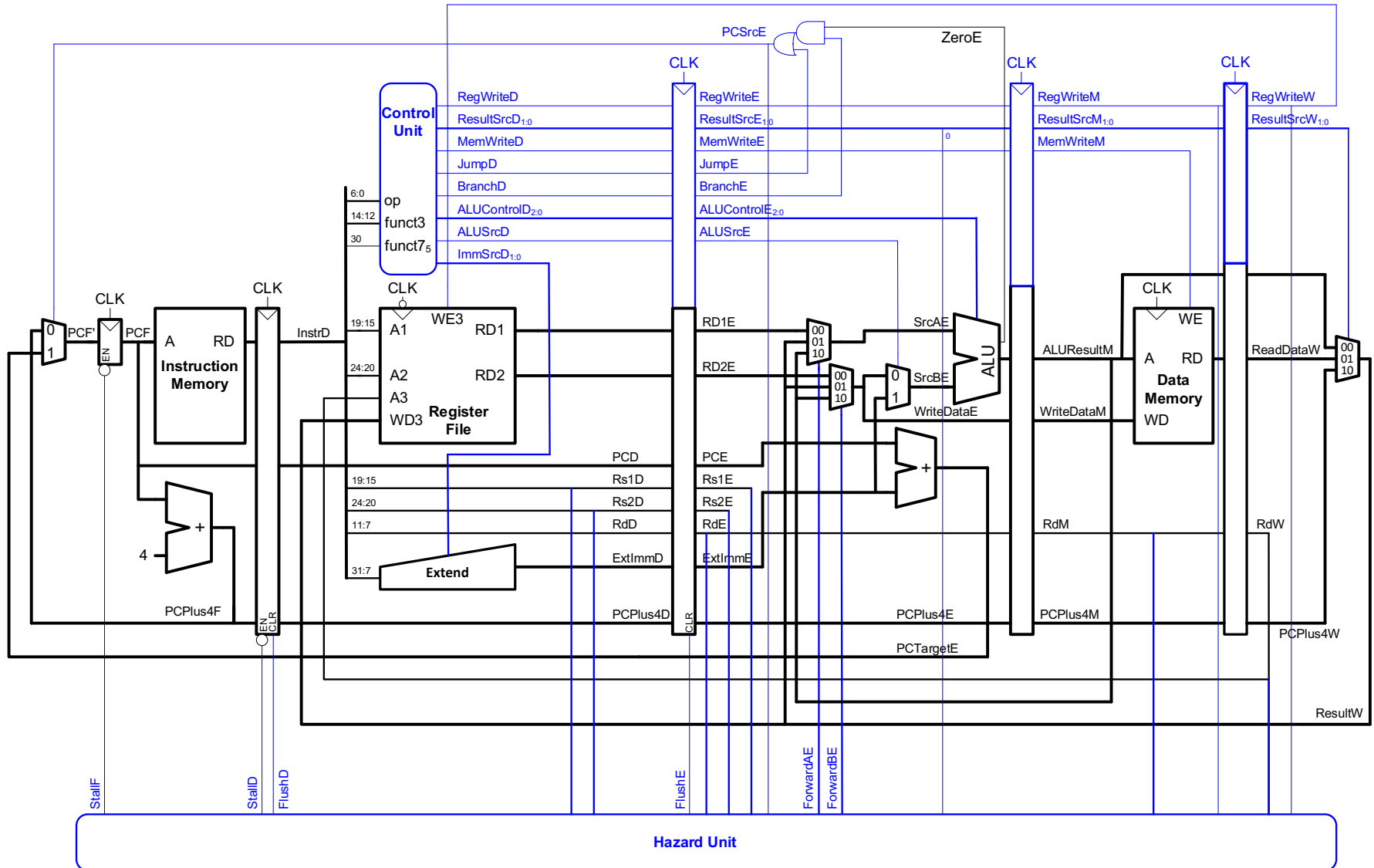RISC-V Pipelined Processor with Hazard Unit



Summary of Hazard Logic

Data hazard logic (shown for SrcA of ALU):

```
if      ((Rs1E == RdM) AND RegWriteM) AND (Rs1E != 0)    // Case 1
        ForwardAE = 10
else if ((Rs1E == RdW) AND RegWriteW) AND (Rs1E != 0)    // Case 2
        ForwardAE = 01
else    ForwardAE = 00                                     // Case 3
```

Load word stall logic:

```
lwStall = ((Rs1D == RdE) OR (Rs2D == RdE)) AND ResultSrcE0
StallF = StallD = lwStall
```

Control hazard flush:

```
FlushD = PCSrcE
FlushE = lwStall OR PCSrcE
```


Advanced Microarchitecture

Advanced Microarchitecture

- Deep Pipelining
- Micro-operations
- Branch Prediction
- Superscalar Processors
- Out of Order Processors
- Register Renaming
- SIMD
- Multithreading
- Multiprocessors

Deep Pipelining

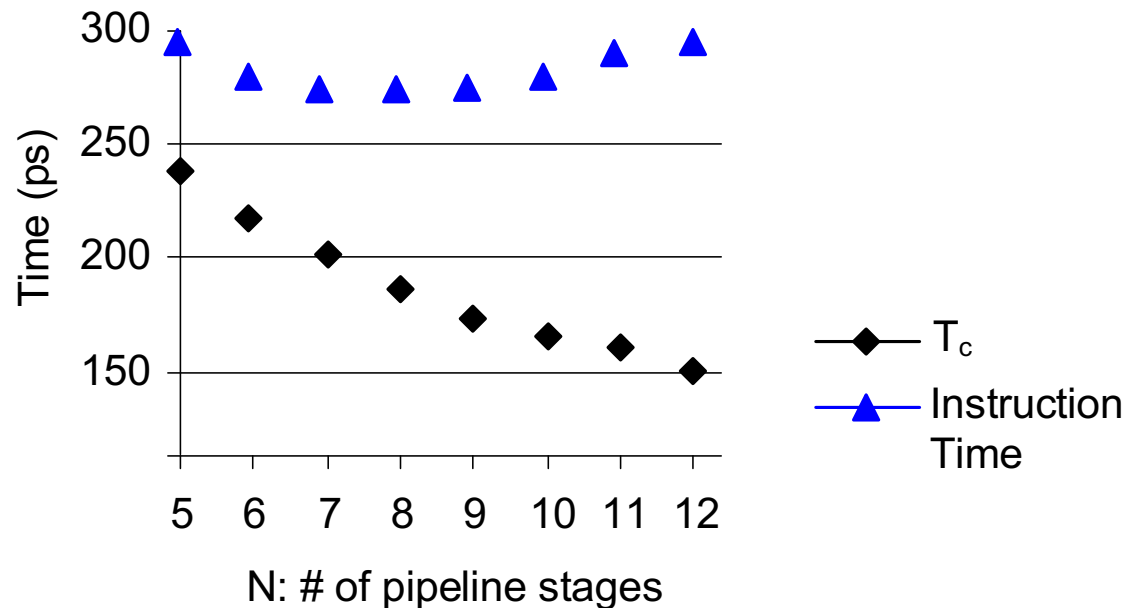- **10-20 stages typical**
- Number of stages limited by:
 - Pipeline hazards
 - Sequencing overhead
 - Power
 - Cost



Micro-operations

- Decompose complex instructions into series of simple instructions called ***micro-operations*** (*micro-ops* or μ -ops)
- **At run-time**, complex instructions are decoded into one or more micro-ops
- Used heavily in **CISC** (complex instruction set computer) architectures (e.g., x86)

Complex Op

```
lw s1, 0(s2), postincr 4
```

Micro-op Sequence

```
lw    s1, 0(s2)
addi  s2, s2, 4
```

Without μ -ops, would need 2nd write port on the register file

Branch Prediction

- **Guess** whether branch will be taken
 - Backward branches are usually taken (loops)
 - Consider history to improve guess
- Good prediction **reduces fraction of branches requiring a flush**

Branch Prediction

- Ideal pipelined processor: $CPI = 1$
- Branch misprediction increases CPI
- **Static branch prediction:**
 - Check direction of branch (forward or backward)
 - If backward, predict taken
 - Else, predict not taken
- **Dynamic branch prediction:**
 - Keep **history** of last several hundred (or thousand) branches in *branch target buffer*, record:
 - Branch destination
 - Whether branch was taken

Dynamic Branch Prediction

- 1-bit branch predictor
- 2-bit branch predictor

Branch Prediction Example

```
addi s1, zero, 0      # s1 = sum
addi s0, zero, 0      # s0 = i
addi t0, zero, 10     # t0 = 10
```

```
For:                  # for (i=0; i<10; i=i+1)
    bge s0, t0, Done
    add s1, s1, s0     # sum = sum + i
    addi s0, s0, 1     # i = i + 1
    j For
```

```
Done:
```

1-Bit Branch Predictor


- **Remembers** whether branch was taken the last time and **does the same thing**
- Mispredicts first and last branch of loop

```
addi s1, zero, 0      # s1 = sum
addi s0, zero, 0      # s0 = i
addi t0, zero, 10     # t0 = 10
```

```
For:                  # for (i=0; i<10; i=i+1)
    bge s0, t0, Done
    add s1, s1, s0     # sum = sum + i
    addi s0, s0, 1     # i = i + 1
    j For
```

Done:

2-Bit Branch Predictor

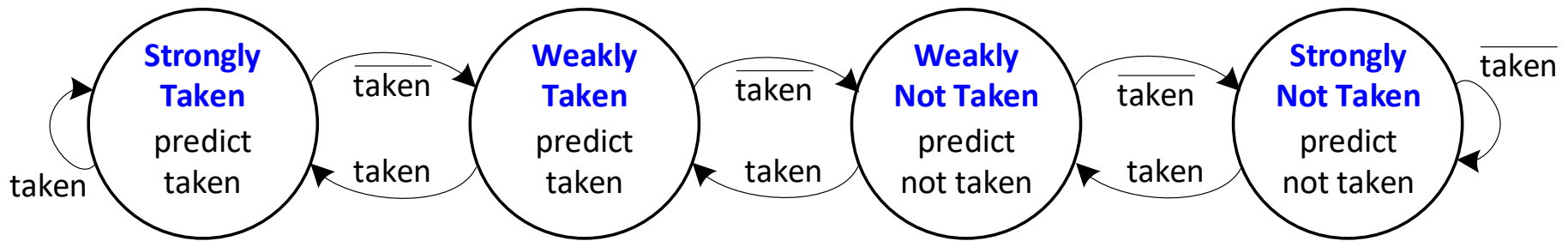

```
addi s1, zero, 0      # s1 = sum
addi s0, zero, 0      # s0 = i
addi t0, zero, 10     # t0 = 10
```

```
For:                  # for (i=0; i<10; i=i+1)
    bge s0, t0, Done
    add s1, s1, s0     # sum = sum + i
    addi s0, s0, 1     # i = i + 1
    j    For
```

Done:

Only mispredicts **last branch** of loop