

# Experiment 4 - Accelerator and Wrappers

Student Name : Shahzad Momayez , Mohammad Amanluo

Student ID : 810100272 , 810100084

**Abstract** — This document is a student report to experiment #4 of Digital Logic Laboratory course at ECE Department, University of Tehran. The goal of this experiment is to design an accelerator and wrapper and experiment how accelerators can increase the performance of our work.

**Keywords** — Accelerator and Wrappers

## I. INTRODUCTION

Chip is an integrated circuit that integrates multiple components including digital, analog, hardware and software programs all in a single chip. The main core of an SoC is a processor that handles different computational tasks within the system. In addition to the processor, the system includes a memory, Input/Output ports and accelerators.

The main task work of an SoC(system on chip) is a processor that handles different computational tasks within the system. In addition to the processor, the system includes a memory, Input/ Output ports and accelerators. Accelerator does a single task with a high frequency which is contrary to CPU. To increase the speed of an SOC, hardware accelerators are usually embedded in the system. The processor will dispute some of its tasks to the hardware accelerator and during this time the accelerator performs several of the same or different operations and store the result values in a memory. The CPU will access these results when it finishes its tasks. The focus of this experiment is on Accelerators and how to integrate them in an SOC. Figure 1 shows the block diagram of a typical Embedded system including a processor, an accelerator and a memory.

 


Figure 1: Block diagram of a typical integrated circuit

## II. Design

Any components that is in communication with CPU talks to CPU via signals "start" and "done". The embedded system shown in this figure works as follows: When the CPU needs to compute an exponential value, because of the higher estimation speed of accelerator it asks the exponential hardware accelerator to complete this task. In this way the CPU can complete other software tasks in parallel with the accelerator. Before starting the computation, the CPU should send a set of data from memory to the accelerator. This data will be stored in a buffer inside the accelerator. When transferring is finished, CPU initiates the accelerator for an N round exponential estimation. CPU uses its address bus for initiating a component. By decoding, the address bus through an address logic as shown in figure 1, accelerator will have its "start" signal issued when needed. For simplicity in this experiment you will implement the whole CPU and address logic inside the test bench and when implementing on an FPGA, you will feed "start" through board switches.

 


Figure 2: Block diagram of exponential accelerator

In this experiment we implement 3 main parts:

- Exponential Accelerator Engine
- Exponential Accelerator Wrapper
- Implementing Accelerator on FPGA

## III. Exponential Engine

this module receives a 16-bit input "x" and generates an 16-bit output "Fractionalpart" and 2-bit "Integerpart". The accelerator starts working with a complete pulse on signal "start" and when the computation is completed signal "done" will be sent to the processor to acknowledge it.

Here are some of the formulas we used in this experiment:

$$e^{x_i} = 2^{u_i} \cdot e^{v_i}$$

$$e^{x_i} = e^{v_i} \ll u_i \quad u_i = \left\lfloor z_i \cdot \log_2 e \right\rfloor$$

$$e^{x_i} = \begin{cases} e^{v_i} \ll u_i \\ e^{2 \cdot v_i} \ll u_i \\ \dots \\ e^{2^{(n-1)} \cdot v_i} \ll u_i \end{cases} \begin{cases} \text{if } v_i < 1/2^{(n-1)} \\ \text{if } u_i < x_i < u_i + 1 \end{cases}$$

 


Fig3. Block diagram of exponential accelerator

Here are the Verilog of the project :

```
module exponential(input clk,rst,start, input [15:0] x,
                  output done, output [1:0] intpart, output [15:0]fracpart);

    wire co,zx,initx,ldx,st,initl,ldt,zr,initr,ldr,zc,ldc,enc,s;

    controller control(clk,rst,start,co,done, zx,initx,ldx,
                      st,initl,ldt, zr,initr,ldr, zc,ldc,enc, s);

    datapath dP(clk,rst, zx,initx,ldx, st,initl,ldt,
                zr,initr,ldr, zc,ldc,enc, s,x,co,[intpart,fracpart]);

endmodule

`timescale 1 ns/ 1 ns
module expTB;
    reg clk, rst, start;
    reg [15:0] x;
    wire done;
    wire [1:0] intpart;
    wire [15:0] fracpart;

    exponential expEng(clk ,rst , start, x, done, intpart, fracpart);

    always #5 clk = ~clk;
    initial begin
        rst = 1'b1;
        clk = 1'b0;
        start = 1'b0;
        #10 start = 1'b1;
        #10 x = 0;
        #5 rst = 1'b0;
        #40 start = 1'b0;
        #10000;
        #50 x = 16'b0100000000000000;
        #1000 start = 1'b1;
        #20 start = 1'b0;
        #10000;
        #50 x = 16'h8000;
        #1000 start = 1'b1;
        #20 start = 1'b0;
        #30000 $stop;
    end
endmodule
```

Fig 4. Verilog of exponential engine

 


Fig5. X=00  
 $e^0=1 \sim 00.1111111111111111$

 


Fig6. X=2<sup>-2</sup> = 0.25  
 $e^{0.25} = 1.28402541$

 


Fig7. X=2<sup>-1</sup> = 0.5  
 $e^{0.5} = 1.648721270 \sim 01.1010011000001011$

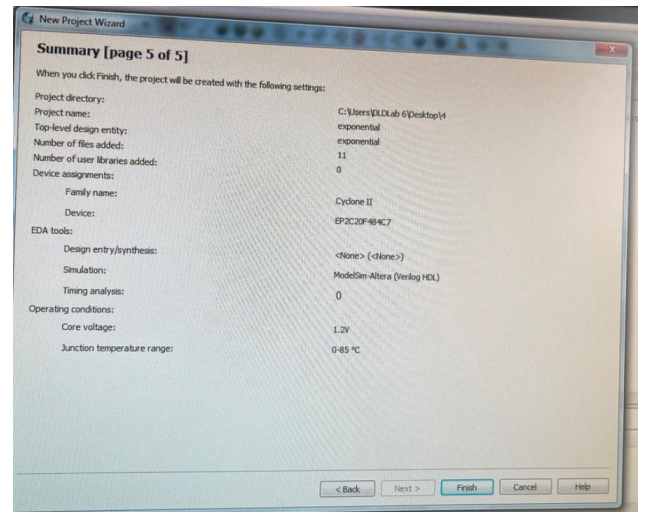


Fig8. summery

Flow Summary	
Flow Status	Successful - Mon Apr 24 14:10:47 2023
Quartus II 32-bit Version	12.1 Build 177 11/07/2012 SJ Web Edition
Revision Name	exponential
Top-level Entity Name	exponential
Family	Cyclone II
Device	EP2K10K10-10
Timing Models	Final
Total logic elements	101 / 18,752 (< 1 %)
Total combinational functions	100 / 18,752 (< 1 %)
Dedicated logic registers	60 / 18,752 (< 1 %)
Total registers	60
Total pins	38 / 315 (12 %)
Total virtual pins	0
Total memory bits	0 / 239,616 (0 %)
Embedded Multiplier 9-bit elements	2 / 52 (4 %)
Total PLLs	0 / 4 (0 %)

Fig9. Flow summary

Slow Model Fmax Summary			
Fmax	Restricted Fmax	Clock Name	Note
110.51 MHz	110.51 MHz	clk	

Fig 10 . max frequency of module

The figure above shows the synthesis result in Quartus II Software. It shows that the maximum frequency that this module can operate is 110.51 MHz

#### IV. Exponential Accelerator Wrapper

We know that the accelerator works with a higher frequency than the processor, for the handshaking signals of "start" and "done" the accelerator have to wait for the processor to send and receive these signals with its low frequency. This imposes some timing overhead to the accelerator and hence performance reduction. In order to use this free time, the accelerator can calculate multiple exponential values. Each input value is split into an integer number  $z_i$  and a fractional number  $v_i$  as below:

$$x_i = z_i + v_i$$

$$e^{x_i} = e^{z_i} \cdot e^{v_i}$$

we calculate the exponential part by shifting to the left. the wrapper receives single input in the form of a fractional value,  $v_i$ , and an integer value  $u_i$  and a start signal from processor.

 


Figure 11: Wrapper for exponential accelerator

In order to shift the output of exponential engine, a combinational shifter is required. The input of this shifter is the  $u_i$  value that is provided outside the wrapper. To store the value of  $u_i$ , a register called  $u_{ireg}$  is used.

When an exponential value is calculated then it should be stored in a FIFO so when the CPU finishes it's work it can retrieve all the results. When all calculations are finished the controller sends a done signal on the wrapper output.

 


Fig12. controller

```

define Idle 3'b000
define Init 3'b001
define Begin 3'b010
define Eng_start 3'b011
define mult 3'b100
define done 3'b101
define Shift 3'b110

module counter_ctrl (input clk, rst, zero, ld, enb, input [2:0] in ,output reg [3:0] out, output co):
    always@(posedge clk, posedge rst)begin
        if(rst == 1'b1)
            out <= 0;
        else
            if(zero == 1'b1)
                out <= 0;
            else if(ld == 1'b1)
                out <= in;
            else if(enb == 1'b1)
                out <= out + 1'b1;
            end
        assign co = (out >= 4'b1000)? 1'b1: 1'b0;
    endmodule

```

```

module cu(input start,clk,rst,eng_done,
output reg done,reset,ld,ui_reg_ld,eng_start,wr_reg,cnt_en,sh_en);
    reg[2:0] ps,ns;
    reg[1:0] count;
    reg co;
    always@(posedge clk , posedge rst)begin
        if(rst) begin
            ps<='Idle;
        end
        else
            ps<='ns;
        end
    end
    always@(ps ,start,eng_done,co)begin
        case(ps)
            'Idle: ns = start?'Init':'Idle;
            'Init: ns = start?'Init':'Begin;
            'Begin: ns = 'Eng;
            'Eng: ns = 'Mult;
            'Mult: ns = eng_done?'Done':'Mult;
            'Done: ns = co?'Idle':'Shift;
            'Shift: ns = 'Eng;
            default ns='Idle;
        endcase
    end
    always@(ps)begin
        (done,reset,ld,ui_reg_ld,eng_start,wr_reg,cnt_en,sh_en) = 0'b00000000;
        case(ps)
            'Idle : done = 1;
            'Init : reset = 1;
            'Begin : begin ld = 1; ui_reg_ld=1; end
            'Eng : eng_start=1;
            'Done : begin wr_reg=1;cnt_en=1; end
            'Shift : sh_en =1;
        endcase
    end
    always@(posedge cnt_en , posedge rst)begin
        if(rst){co ,count} = 3'b000;
        else {co ,count} = count +1;
    end
endmodule

```

Fig13. Controller verilog

```

|timescale 1 ns/ 1 ns
module cntlerTB;
    reg start,rst,eng_done;
    reg clk = 0;
    wire done,reset,ld,ui_reg_ld,eng_start,wr_reg,cnt_en,sh_en;

    cu c(start,clk,rst,eng_done,done,reset,ld,ui_reg_ld,eng_start,wr_reg,cnt_en,sh_en);

    always #1 clk = ~clk;
    initial begin
        #5 rst = 1'b1;
        #5 rst = 1'b0;
        #5 start = 1'b1;
        #5 start = 1'b0;
        #5 eng_done = 1;
        #30 $stop;
    end
endmodule

```

Fig14. Controller testbench

 


Fig15 . wave form

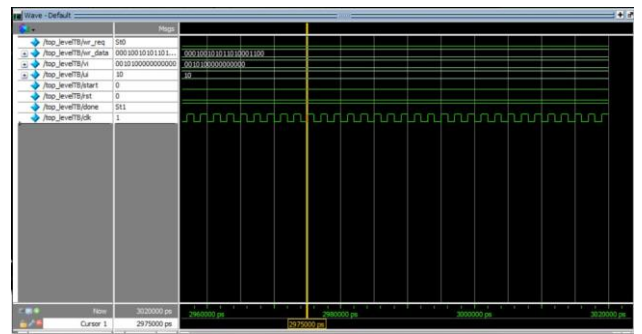


Fig16. ui= 10 =(2)d

$$vi=0010100000000000=0.03125+0.12500=0.15625$$

$$\text{expected : } 4 * e^{(0.15625)} = 4.67647378468$$

$$\text{achived: } 100.101011010001100 = 4.677734375$$

 


Fig17. ui= 11 =(3)d

$$vi=1110000000000000=0.5+0.25+0.12500=0.875$$

$$\text{expected : } 8 * e^{(0.875)} = 19.1910023517$$

$$\text{achived: } 10011.0011000010011000 = 19.1904296875$$

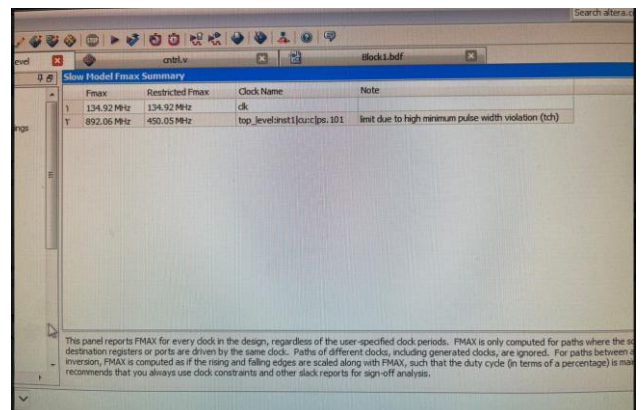


Fig 18 . frequency is shown in the picture above







 


Fig 27.

 


Fig28.

 


Fig29. FPGA implementation

## VI.CONCLUSIONS

All in all, we designed these acclator and wrapper and we implemented our work on FPGA.

## ACKNOWLEDGMENT

This report was prepared and developed by Shahzad Momayez(SID:810100272) and Mohammad Amanlou(SID:810100084), bachelor students of Computer engineering at University of Tehran, under the supervision of Professor Zain Navabi.